

Dc-Dc converter Basics:

KCL \equiv Kershof current law


$$\begin{array}{c} i_2 \\ \swarrow \\ i_1 \\ \searrow \\ i_3 \end{array} \Rightarrow \sum_j i_j = 0$$

what will happen if we Take ^{Time} avg current $\equiv \langle \sum_j i_j \rangle = 0$
well because we know that avg over Time \equiv integral
we can change The order of The integral $\Rightarrow \sum_j \langle i_j \rangle = 0$


\Rightarrow average current into a node $= 0$ $\ominus \Rightarrow$ make sense

same For KVL $\sum_k \langle V_k \rangle = 0$ sumation of avg voltage in Terminals
around a loop $= 0$


PSS \Rightarrow Periodic Steady State.

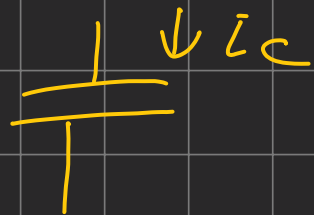

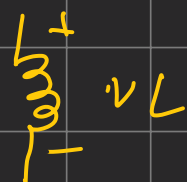
$$\langle i_c \rangle = 0 = C \left[\frac{dv}{dt} \right] \rightarrow 0 \text{ in Steady State}$$


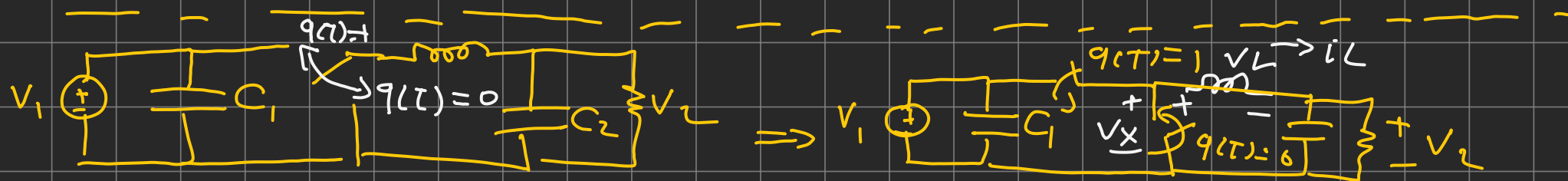
$$\langle v_L \rangle = 0 = L \left[\frac{di}{dt} \right] \rightarrow 0 \text{ in Steady State}$$



Periodic switching:

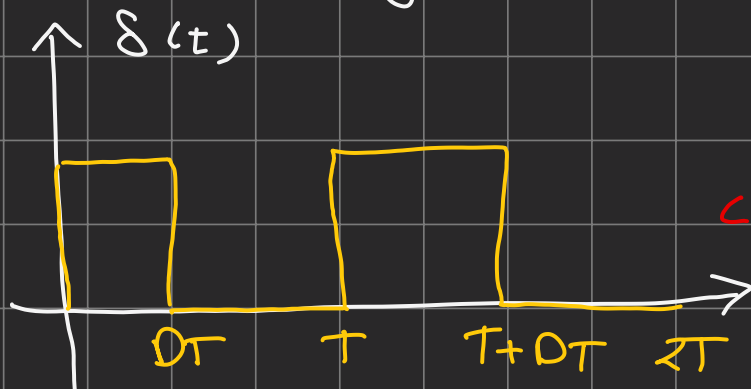


$$V_x - V_L - V_2 = 0$$

$$\langle V_x \rangle - \langle V_L \rangle - \langle V_2 \rangle = 0$$

$\rightarrow 0$ in PSS

$$\langle V_2 \rangle = \langle V_x \rangle$$

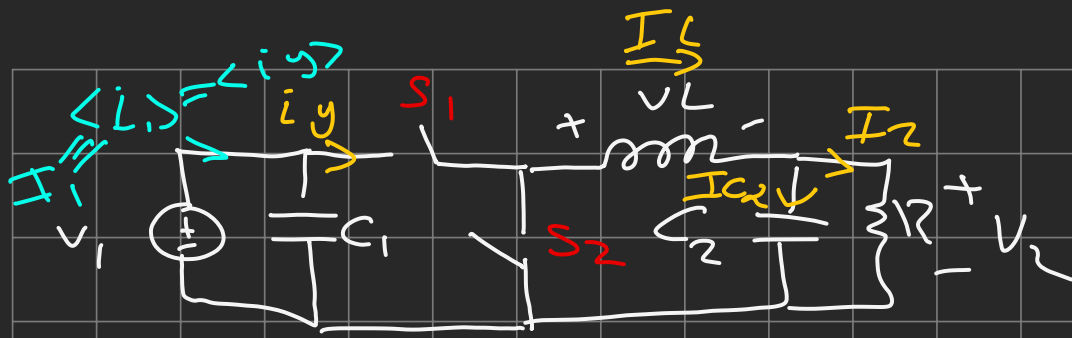
$$\langle V_x \rangle = D \cdot V_1 = \langle V_2 \rangle = D \cdot V_1 \Rightarrow D = 1$$



$$i_L(t) \approx I_L DC$$

=> assumption inductor & capacitor are very big #
 zero voltage ripple
 zero current ripple
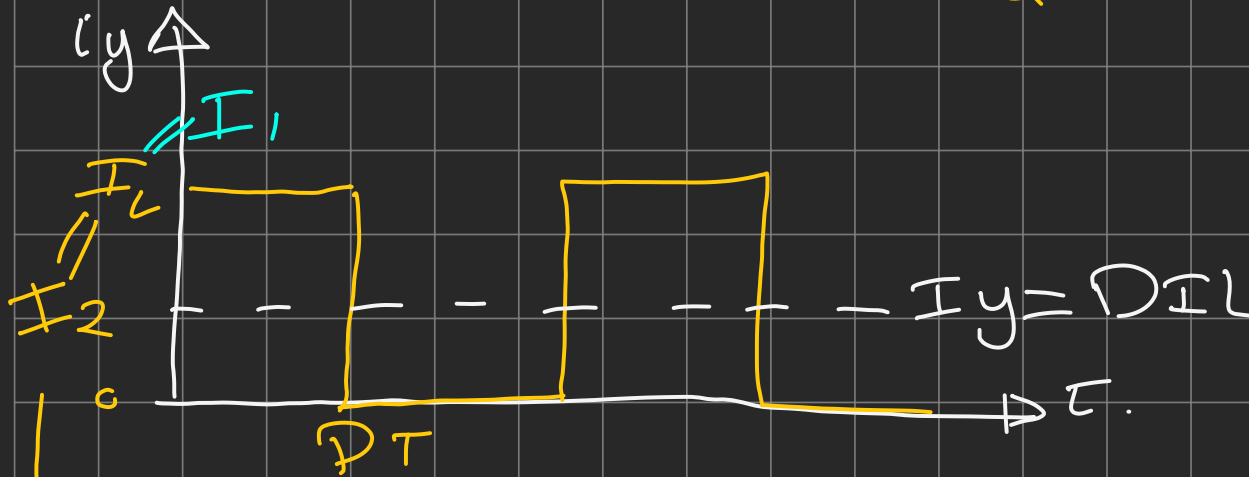
$$V_1(t) = V_1 DC \quad V_2(t) = V_2 DC$$



> why $\langle I_L \rangle = \langle I_2 \rangle + \langle I_{C2} \rangle$
 $\langle I_L \rangle = \langle I_2 \rangle$ (at PSS)

$$I_1 = D I_2$$

$$\Rightarrow \textcircled{2}$$

$$V_2 = D V_1 \Rightarrow \checkmark$$

$$P_{out} = V_2 \cdot I_2 = D V_1 \cdot \frac{I_1}{D} = V_1 I_1$$

Power conservation \neq
No power loss in converter

this converter can step down voltage \Rightarrow [Buck] \neq

how to implement:




on/off

in off state

The inductor want to resist the sudden change so it generate a back EMF \Rightarrow voltage spike \Rightarrow old / new reverse / forward

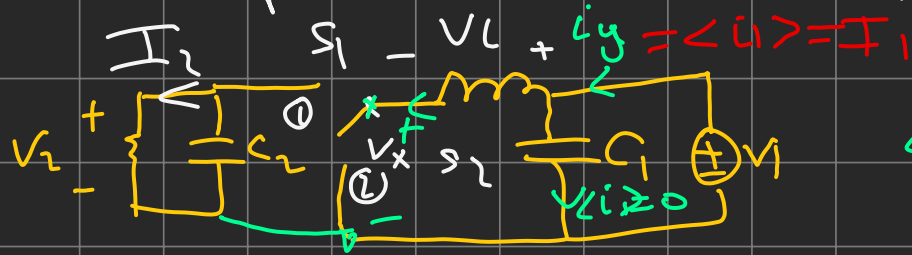Diode provide an alternative path for current to flow






$$\langle V_1 \rangle - \langle V_L \rangle - \langle V_x \rangle = 0$$


$$\langle V_1 \rangle = \langle V_x \rangle$$

$$V_x = \frac{V_1}{1-D} = [1-D] V_2$$

$$V_2 = \frac{V_1}{1-D}$$

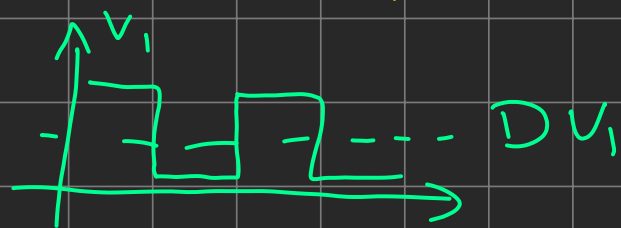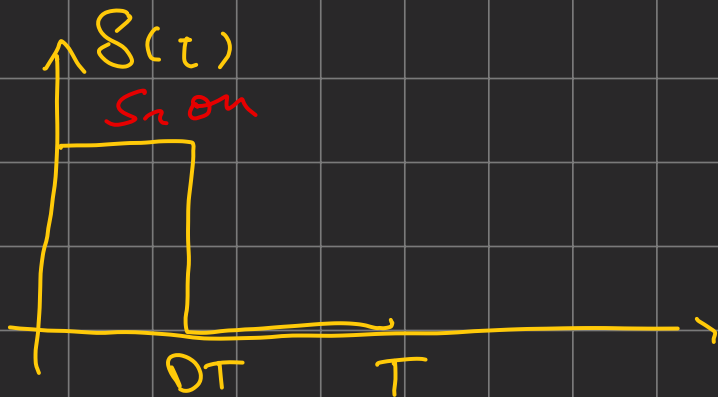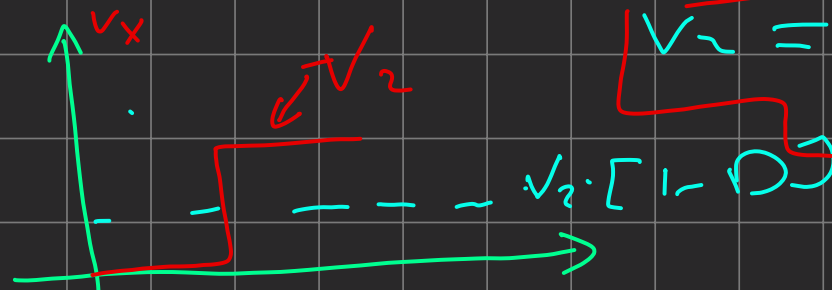

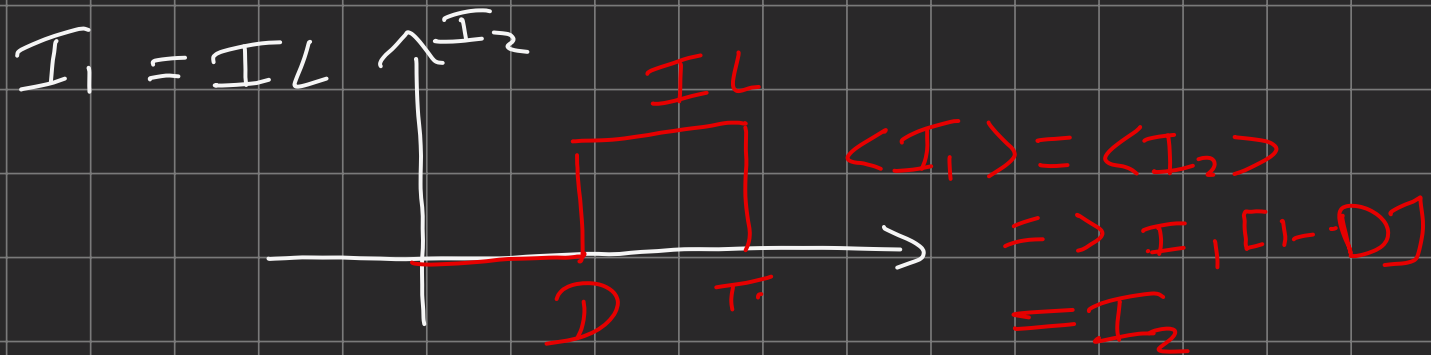
$V_1 < V_2 < \infty \Rightarrow$ Boost DC-DC-converter



$$I_2 = [1-D] I_1$$


$$V_2 = \frac{V_1}{1-D}$$

Boost converter :

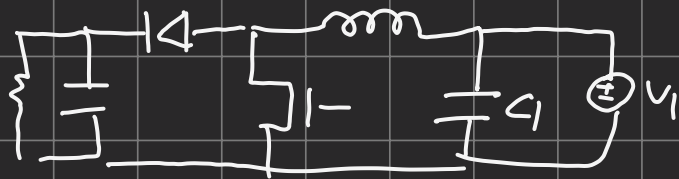

How is IT really working?

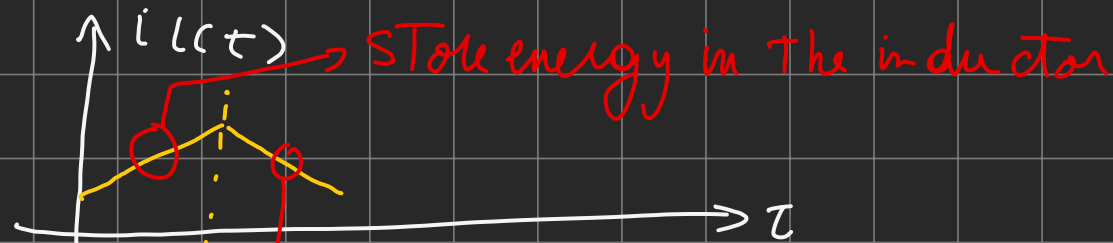Well, let's make some assumption first \Rightarrow inductor is not very big
so



$\rightarrow V_2 > V_1$ -ve voltage drop on inductor
inductor is discharged in the output